

1. Two three-phase load are connected in parallel: 50 kVA at a power factor of 0.9, leading and 125 kVA at a power factor of 0.85, lagging.

Draw the power triangle and determine the combined power factor.

- [illegible]

4. A 460-V, three-phase, 60-Hz source is supplying power to an induction motor. The motor, rated at 60 hp, and 890 rpm, and is operating at rated load with an efficiency of 92.7% and a power factor of 83.5% lagging. Determine
- (a) active power in;
  - (b) apparent power in;
  - (c) power factor angle
  - (d) reactive power.

5. Part 1 A balanced three-phase load, draws 153 A from a 460-V, 60-Hz source, and has a power factor of 60%. Determine
- (a) the apparent power of the load;
  - (b) active power of load;
  - (c) reactive power of load;
  - (d) power-factor angle of load.

Part 2: We want to install a three-phase capacitor bank to correct the system power factor of 95%. Determine:

- (e) new power-factor angle of system;
- (f) new system vars;
- (g) kvar rating of a three-phase capacitor bank required to make this correction;
- (h) capacitance of each branch of the bank if the capacitors are delta connected;
- (i) capacitance of each branch of the bank if the capacitors are wye connected.